



## **$\mu$ Project #3 “A Turn at the Wheel”**

Due Tuesday 2/7

HCI-833 Applied Gadgets,  
Sensors and Activity  
Recognition in HCI  
Spring 2017

---

### **Purpose**

This  $\mu$ project explores the use of a potentiometer to control a simple display.

### **What to Build**

Build a simple device which lights four LEDs one after the other and controls the speed at which the sequence displays with a potentiometer. When the potentiometer is turned fully counter clockwise the LED sequence should proceed slowly. When the potentiometer is turned in the clockwise direction it should proceed faster and faster.

### **Turning the Assignment In and Grading**

This assignment is turned in by having one of your classmates certify completion and turn in a “peer demo” sheet signed by them (and fill out the corresponding on-line form on the Blackboard system as well). This project is pass/fail.  $\mu$ Projects will be accepted without late penalty until Monday April 3<sup>rd</sup> (after which a 10% per day late penalty will be applied). However, please keep in mind that additional  $\mu$ projects will be coming in rapid sequence (and you only have one breadboard to put your circuits on), so don't fall behind.

**Note:**  $\mu$ Project #4 will build on this project, so don't tear down your project after it's been graded.